

## Question Completion Status:

- a. inductance
- b. reactance
- c. resistance
- d. henrys

**QUESTION 8****1 points**

Saved

In a pure inductive circuit, current

- a. lags voltage by  $90^\circ$
- b. is in phase with voltage
- c. leads voltage by  $90^\circ$
- d. lags voltage by  $180^\circ$

**QUESTION 9****1 points**

Saved

The power calculated for a pure inductance is stated in units of

- a. joules
- b. watts
- c. volt amperes
- d. reactive power

**QUESTION 10****1 points**

Saved

When current flows in a conductor, a magnetic field is created. The magnetic field cuts the conductor which creates a voltage in the conductor. This voltage is called \_\_\_\_ voltage.

- a. inductive
- b. induced
- c. applied
- d. conducted

**QUESTION 11****1 points**

Saved

The symbol for inductive reactance is

- a. H
- b. R
- c.  $X_L$
- d.  $X_C$

